

## Activity: Boolean to Logic Diagram and Truth Table

Total: 3 Problems (5 points each = 15 points)

---

### Problem# 1 (5 pts)

Given:

$$F_1 = A \cdot B + A \cdot B'$$

1.

A

$$\begin{aligned} &A \cdot B + A \cdot B' \\ &= A \cdot (B + B') \\ &= A \cdot 1 \\ &F_1 = A \end{aligned}$$

B

$$A \rightarrow F$$

C

A	B	F1
0	0	0
0	1	0
1	0	1
1	1	1

**Problem 2 (5 pts)**

**Given:**


$$F_2 = (A + B) \cdot (A' + C)$$

1

A

$$\begin{aligned} & (A+B) \cdot (A' + C) \\ &= (A+B) \cdot A' (A+B) \cdot C \\ &= (A \cdot A' + B \cdot A') + (A \cdot C + B \cdot C) \\ &= (0 + BA') + (AC + BC) \\ &= BA' + AC + BC \end{aligned}$$

B

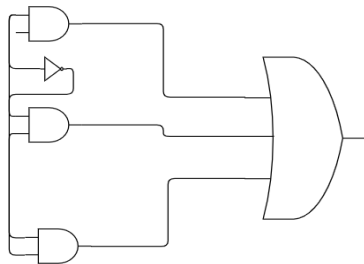

C

A	B	C	F2
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

**Problem 3 (5 pts)**

**Given:**

$$F_3 = (A \cdot B') + (A' \cdot C)$$

A

No need to simplify haha

C

A	B	C	F3
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	0
1	1	1	0